# Lab workshop on FPGA Architecture and programming using Verilog fpga0722

Name: Arpita Nath


## Verilog code:


```
`timescale 1ns / 1ps
module miniproject(
input clk,
//input i0,input i1,input i2,input i3,
//output reg[3:0] y,
output reg[3:0] Y
//output [1:0] count
);
//MUX4to1:
wire [1:0] count;
//wire dat;
wire [3:0] y;
c_counter_binary_2 your_instance_name (
.CLK(clk), // input wire CLK
.Q(count) // output wire [1:0] Q
);
assign dat=count[1] ? (count[0] ? i3 : i2) : (count[0] ? i1 : i0);
//D Latch:
decoder_2x4 decoder (count, dat, y);
always@(*)
if(clk)
Y<=y;
```

```
ila_0 your_result (
.clk(clk), // input wire clk
.probe0(Y) // input wire [3:0] probe0
);
vio_1 your_input_name (
.clk(clk), // input wire clk
.probe_out0({i3,i2,i1,i0}) // output wire [3 : 0] probe_out0
);
endmodule
//2x4Decoder:
module decoder_2x4(
input [1:0] in,
input en,
output reg [3:0] out
);
always@(*)
if(en)
case(in)
0:out = 1;
1:out = 2;
2:out = 4;
3:out = 8;
default: out = 0;
endcase
else
out = 0;
```


#### endmodule

#### **Waveforms**

 


 

When the input is 4'b0110:

 

### When the input is 4'b1010:

 

When the input is 4'b1011:

